

Lab 2 Write-up

1. Introduction:

- a. We modeled our implementation of the different processor elements after the examples given on TED. The main differences were in our alu and register file. For our alu, we have specialized instructions based on our ISA from lab 1. Our register file is very different, as we used one of the registers as an index into which block of registers we were accessing.

2. Summarize ISA From Lab 1


- a. Our ISA from lab 1 applies the concept of an accumulator ISA by using reg0 as an implicit register. Reg1 is also a special register such that it allows us to switch between different register blocks by changing the value between 0, 1, or 2. Reg1 allows us to support 16 registers instead of 8 registers. The operations supported by our ISA are: branch less than (blt), branch equal (beq), shift left (sl), shift right (sr), shift right pad with overflow (sro), set (set), set immediate (sti), halt (halt), load word (lw), store word (sw), add (add), 2's complement (comp), move (mov), jump (j), and clear overflow (clr).
 - i. blt regX, regY: if $\text{regX} < \text{regY}$ then go to the label stored in reg0
 - ii. beq regX, regY: if $\text{regX} == \text{regY}$ then go to the label stored in reg0
 - iii. sl regX, regY: shift regX left by the value in regY
 - iv. sr regX, regY: shift regX right by the value in regY
 - v. sro regX, regY: shift regX right by the value in regY and pad regX with the value stored in overflow
 - vi. set #: put the number in the instruction into reg0
 - vii. sti regX, #: put the number in the instruction into regX
 - viii. halt: signifies the end of the program and stops program counter from incrementing
 - ix. lw regX: store the memory value of reg0 into regX
 - x. sw regX: Sets the memory value of reg0 with regX
 - xi. add regX: $\text{reg0} = \text{reg0} + \text{regX} + \text{overflow}$
 - xii. comp regX; $\text{regX} = -\text{regX}$
 - xiii. mov regX: Assign regX with value in reg0
 - xiv. j: Jump to label stored in reg0
 - xv. clr: set overflow to 0

3. ALU Operations


- ALU: Comp, Assembly Instruction: comp
- ALU: Add, Assembly Instruction: add
- ALU: Shift right, Assembly Instruction: sr
- ALU: Shift right with overflow, Assembly Instruction: sro
- ALU: Shift left, Assembly Instruction: sl
- The register file has 2 address inputs, 1 write address input, a write bit and 2 address outputs. All of the ALU instructions require the 2 address outputs.

4. Verilog Models


ALU

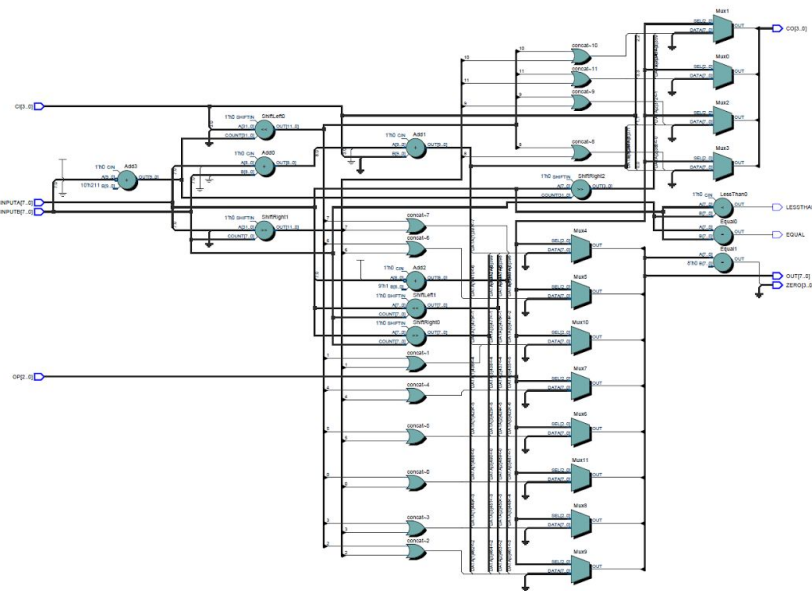


Data_mem

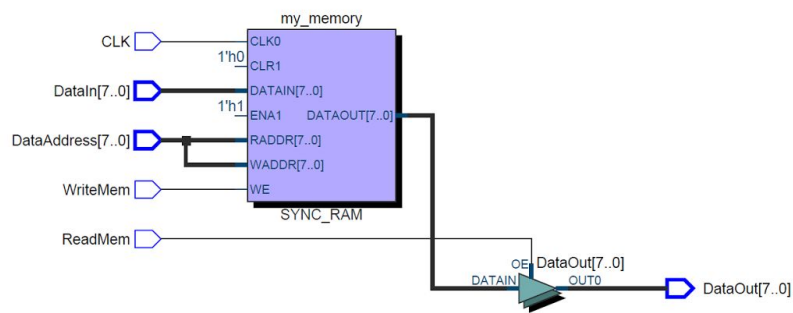


inst_ROM

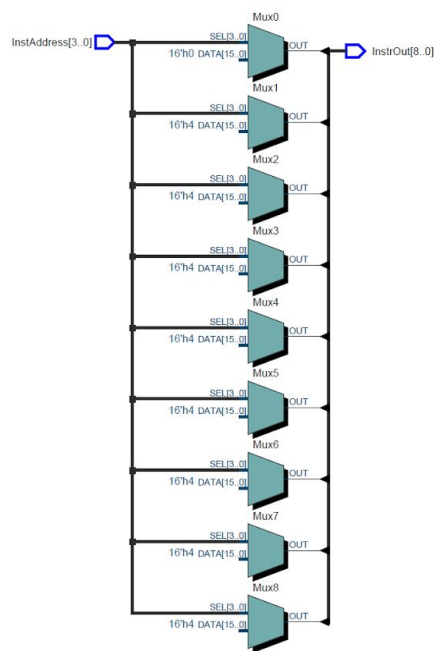

PC

 


Reg_file

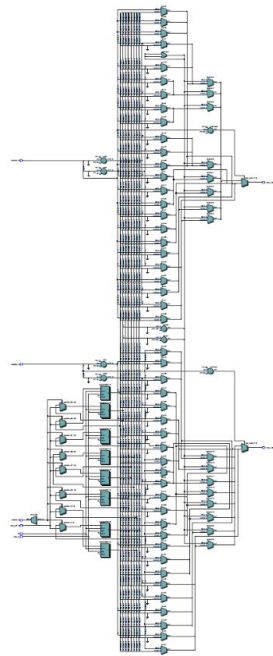


5. Timing Diagrams

- a. Our tests are in the testbench files. We begin with 100ns to initialize everything, then every 20ns after that represents a different test case. (Start at 100000 ps)


PC

 


reg_file

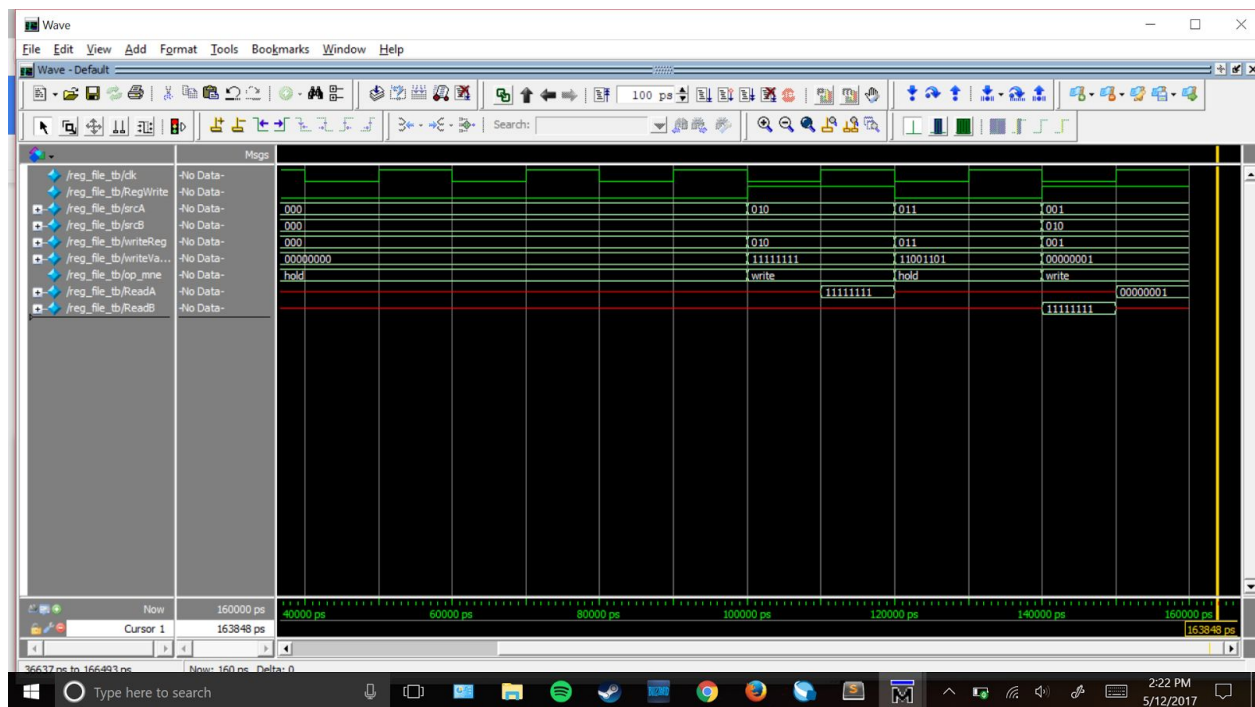


instr_ROM

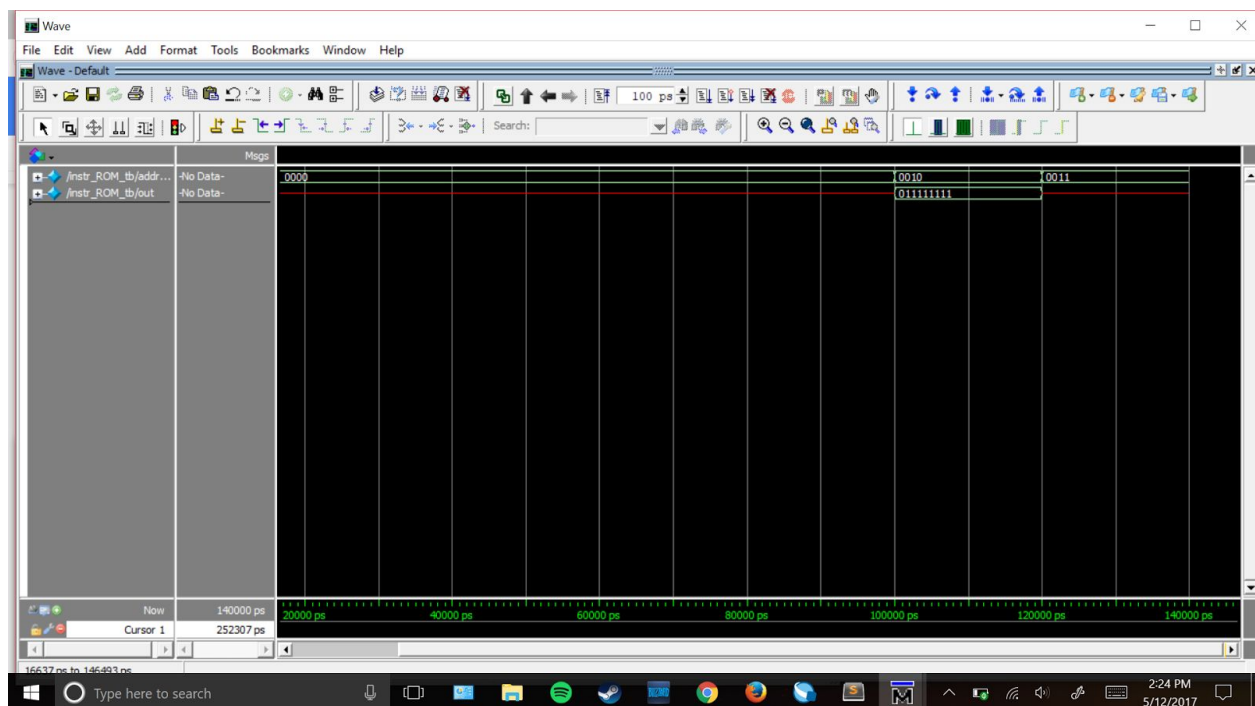

data_mem

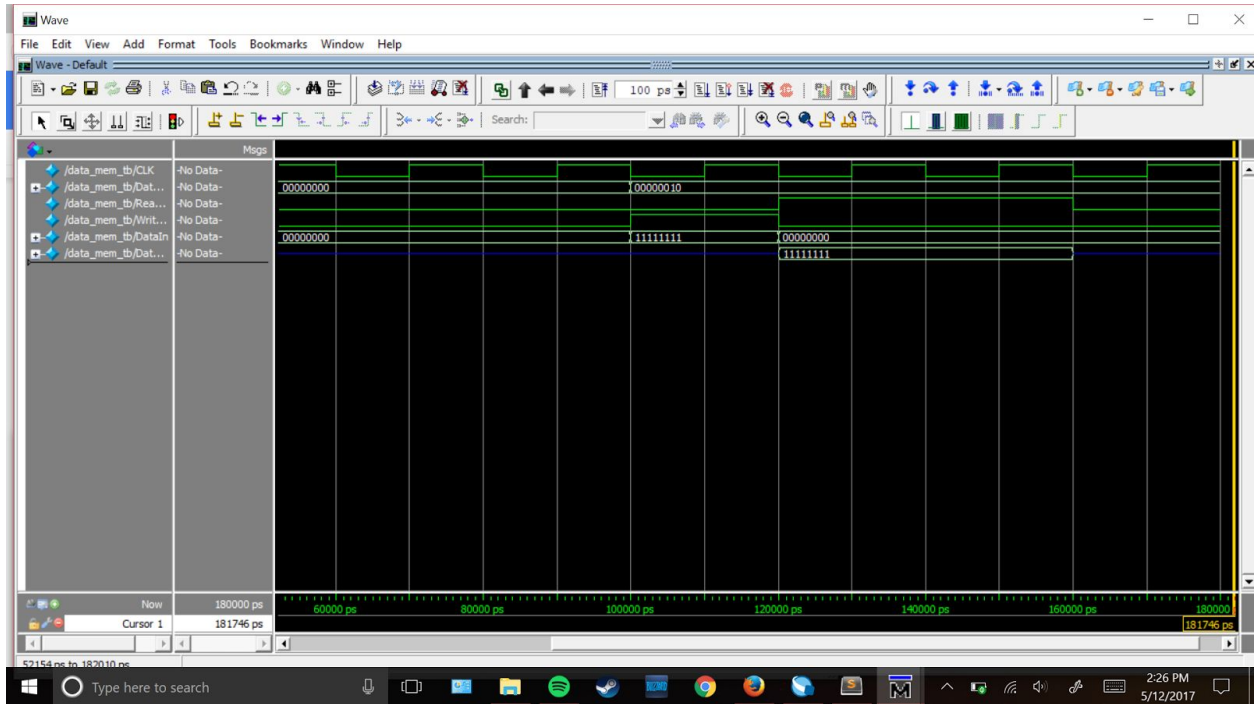

alu

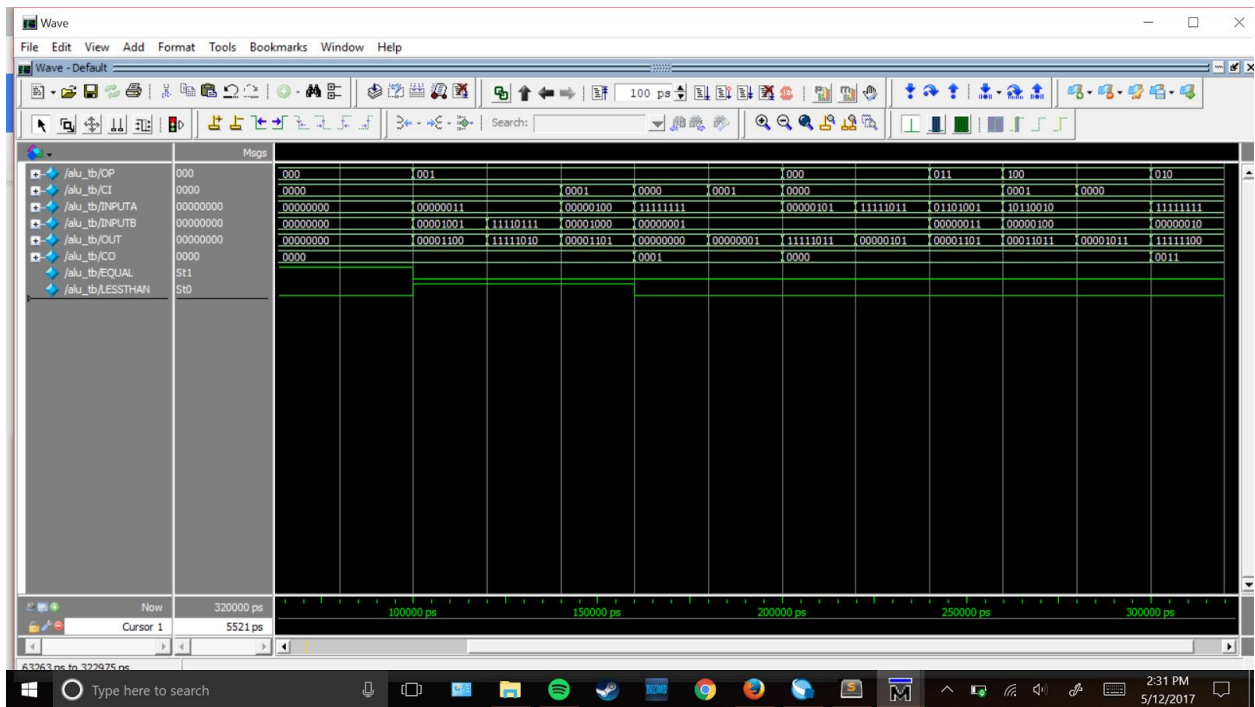

6. Non-arithmetic Instructions

- a. No we do not use the ALU for non-arithmetic instructions. Our branch and jump addresses are stored in reg0 and when a branch is called the program counter will be replaced with whatever is in reg0.

7. Make Fetch Unit Design Easier

- a. The fetch unit consists of the program counter and the instruction memory. To make the program counter design easier, we could take away jumps and branches so the only thing the program counter will do is increment by 1 until a halt is encountered. The instruction memory is just an array that holds all of the instructions so the design is already quite simple in our case.

8. Make ALU Design Easier

- a. The ALU design currently makes heavy use of a carry out, so if we eliminate the carry out our ALU will be a lot simpler. But this would severely impact the different types of complex programs our ISA could perform.

9. Make Register File Design Easier

- a. To make our register file design easier, we could decrease the amount of registers our ISA supports by changing the functionality of reg1. Currently if reg1 = 0 we have access to reg0-reg7, if reg1 = 1 we have access to reg0, reg1, and reg8-reg13, and if reg1 = 2 we have access to reg0, reg1, and reg14-reg15. So we could change reg1 to be a standard register, but this would decrease the amount of registers from 16 to 8.

10. Most Complex Instruction

- a. Add: For our add instruction in the ALU, we add together 2 8-bit registers and a 4-bit Carry In and store it in a 12 bit temp register. We then take the upper 4 MSB of temp and store in Carry Out, and take the lower 8 LSB of temp and store in OUT.

11. Adding Instructions to ALU

- a. Currently to perform a subtract you would have to do a 2's comp and then add the two registers, so instead we could just add a subtract instruction that performs the subtraction in 1 cycle instead of 2. Also we could add an increment instruction to handle the looping variables.